



- ①在Read\_data1与pc间加一个mux用于完成auipc指令
- ②在Branch, jal信号选择器前添加jalr\_PC信号, 用于完成jalr指令
- ③sub指令通路与add指令基本一致
- ④blt指令通路与beq指令基本一致, 只需通过ALUop来区分两个指令

## (2) CPU各模块

### ①rf (寄存器堆)

```
1  module rf#(  
2      parameter m=5,WIDTH=32  
3  )(  
4      input clk,we,rst,  
5      input [m-1:0] wa,  
6      input [m-1:0] ra0,ra1,  
7      input [WIDTH-1:0] wd,  
8      output [WIDTH-1:0] rd0,rd1,  
9      input [m-1:0] rf_addr,  
10     output [WIDTH-1:0] rf_data  
11 );  
12  
13 parameter sum = 8'b1 << m;  
14 reg [WIDTH-1:0] regfile [0:sum-1];  
15  
16 assign rd0 = regfile[ra0], rd1 = regfile[ra1];  
17 assign rf_data = regfile[rf_addr];  
18  
19 always @(posedge clk or posedge rst)  
20 begin  
21     if(rst)  
22     begin  
23         regfile[0] <= 0;  
24         regfile[1] <= 0;  
25         regfile[2] <= 0;  
26         regfile[3] <= 0;  
27         regfile[4] <= 0;  
28         regfile[5] <= 0;  
29         regfile[6] <= 0;  
30         regfile[7] <= 0;  
31         regfile[8] <= 0;  
32         regfile[9] <= 0;  
33         regfile[10] <= 0;  
34         regfile[11] <= 0;  
35         regfile[12] <= 0;  
36         regfile[13] <= 0;  
37         regfile[14] <= 0;  
38         regfile[15] <= 0;  
39         regfile[16] <= 0;  
40         regfile[17] <= 0;  
41         regfile[18] <= 0;  
42         regfile[19] <= 0;  
43         regfile[20] <= 0;  
44         regfile[21] <= 0;  
45         regfile[22] <= 0;
```

```

46         regfile[23] <= 0;
47         regfile[24] <= 0;
48         regfile[25] <= 0;
49         regfile[26] <= 0;
50         regfile[27] <= 0;
51         regfile[28] <= 0;
52         regfile[29] <= 0;
53         regfile[30] <= 0;
54         regfile[31] <= 0;
55     end
56     else if (we && wa!= 0) regfile[wa] <= wd;
57 end
58 endmodule

```

## ②immg (立即数处理模块)

```

1  module immg(
2  input [31:0] ins,
3  output reg [31:0] imm
4  );
5
6  always @(*)
7  begin
8      case(ins[6:0])
9          7'b0000011:
10             begin
11                 imm = {{20{ins[31]}},ins[31:20]}; //lw
12             end
13          7'b0100011:
14             begin
15                 imm = {{20{ins[31]}},ins[31:25],ins[11:7]}; //sd
16             end
17          7'b0010011: imm = {{20{ins[31]}},ins[31:20]}; //addi
18          7'b1100011: imm =
19             {{20{ins[31]}},ins[7],ins[30:25],ins[11:8],1'b0}; //beq,blt
20          7'b1101111: imm =
21             {{12{ins[31]}},ins[19:12],ins[20],ins[30:21],1'b0}; //jal
22          7'b0010111: imm = {ins[31:12],12'b0}; //auipc
23          7'b1100111: imm = {{20{ins[31]}},ins[31:20]}; //jalr
24          default:    imm = 0; //add,sub
25      endcase
26  end
27 endmodule

```

## ③alu模块

```

1  module alu#( parameter WIDTH = 32
2  )(
3      input[WIDTH-1:0] a,
4      input[WIDTH-1:0] b,
5      input [31:0] ins,
6      input [2:0] f,

```

```

7     output reg [WIDTH-1:0] y,
8     output z
9 );
10
11 wire signed [31:0] sa;
12 wire signed [31:0] sb;
13 assign sa = a;
14 assign sb = b;
15
16 always@(*)
17 begin
18     case(f)
19         3'b000: y = a + b;
20         3'b001: y = a - b;
21         3'b010: y = a & b;
22         3'b011: y = a | b;
23         3'b100: y = a ^ b;
24         3'b101: y = (sa>=sb);
25         default: y = 0;
26     endcase
27 end
28
29 assign z = y ? 1'b0 : 1'b1;
30
31 endmodule

```

#### ④alu\_control模块

```

1 module alu_control(
2     input [1:0] aluop,
3     output reg [2:0] sel);
4
5     always@(*)
6     begin
7         case(aluop)
8             2'b01: sel = 3'b001;
9             2'b11: sel = 3'b101;
10            default: sel = 3'b000;
11        endcase
12    end
13 endmodule

```

#### ⑤control模块

```

1 module control(
2     input [31:0] ins,
3     output reg ALUSrc,RegWrite,MemRead,MemWrite,Branch,JUMP,jalr_PC,auipc,
4     output reg [1:0] ALUOp, reg [1:0] MemtoReg
5 );
6
7     always@(*)
8     begin
9         case(ins[6:0])

```

```

10         7'b0110011:
11             begin
12                 if(ins[31:25]==7'b0)    //add
13                     begin
14                         ALUSrc = 0; MemtoReg = 2'b00; RegWrite = 1; MemRead = 0;
15                         MemWrite = 0;
16                         Branch = 0; JUMP = 0; ALUOp = 2'b10; auipc = 0; jalr_PC
17                         = 0;
18                     end
19                 else                    //sub
20                     begin
21                         ALUSrc = 0; MemtoReg = 2'b00; RegWrite = 1; MemRead = 0;
22                         MemWrite = 0;
23                         Branch = 0; JUMP = 0; ALUOp = 2'b01; auipc = 0; jalr_PC
24                         = 0;
25                     end
26             end
27         7'b0000011:    //lw
28             begin
29                 ALUSrc = 1; MemtoReg = 2'b01; RegWrite = 1; MemRead = 1;
30                 MemWrite = 0;
31                 Branch = 0; JUMP = 0; ALUOp = 2'b00; auipc = 0; jalr_PC = 0;
32             end
33         7'b0100011:    //sw
34             begin
35                 ALUSrc = 1; MemtoReg = 2'b00; RegWrite = 0; MemRead = 0;
36                 MemWrite = 1;
37                 Branch = 0; JUMP = 0; ALUOp = 2'b00; auipc = 0; jalr_PC = 0;
38             end
39         7'b0010011:    //addi
40             begin
41                 ALUSrc = 1; MemtoReg = 2'b00; RegWrite = 1; MemRead = 0;
42                 MemWrite = 0;
43                 Branch = 0; JUMP = 0; ALUOp = 2'b10; auipc = 0; jalr_PC = 0;
44             end
45         7'b1100011:    // beq,blt
46             begin
47                 if(ins[14:12]==3'b000)    //beq
48                     begin
49                         ALUSrc = 0; MemtoReg = 0; RegWrite = 0; MemRead = 0 ;
50                         MemWrite = 0;
51                         Branch = 1; JUMP = 0; ALUOp = 2'b01; auipc = 0;
52                         jalr_PC = 0;
53                     end
54                 else                    //blt
55                     begin
56                         ALUSrc = 0; MemtoReg = 0; RegWrite = 0; MemRead = 0 ;
57                         MemWrite = 0;
58                         Branch = 1; JUMP = 0; ALUOp = 2'b11; auipc = 0;
59                         jalr_PC = 0;
60                     end
61             end
62         7'b1101111:    //jal
63             begin
64                 ALUSrc = 0; MemtoReg = 2'b10; RegWrite = 1; MemRead = 0 ;
65                 MemWrite = 0;
66                 Branch = 0; JUMP = 1; ALUOp = 2'b00; auipc = 0; jalr_PC = 0;
67             end

```


```


56         7'b1100111://jalr
57         begin
58             ALUSrc = 1; MemtoReg = 2'b10; RegWrite = 1; MemRead = 0 ;
MemWrite = 0;
59             Branch = 0; JUMP = 0; ALUOp = 2'b00; auipc = 0; jalr_PC =
1;
60         end
61         7'b0010111: //auipc
62         begin
63             ALUSrc = 1; MemtoReg = 2'b00; RegWrite = 1; MemRead = 0 ;
MemWrite = 0;
64             Branch = 0; JUMP = 0; ALUOp = 2'b10; auipc = 1; jalr_PC = 0;
65         end
66         default:
67         begin
68             ALUSrc = 0; MemtoReg = 2'b00; RegWrite = 0; MemRead = 0 ;
MemWrite = 0;
69             Branch = 0; JUMP = 0; ALUOp = 2'b00; auipc = 0; jalr_PC = 0;
70         end
71     endcase
72 end
73 endmodule

```
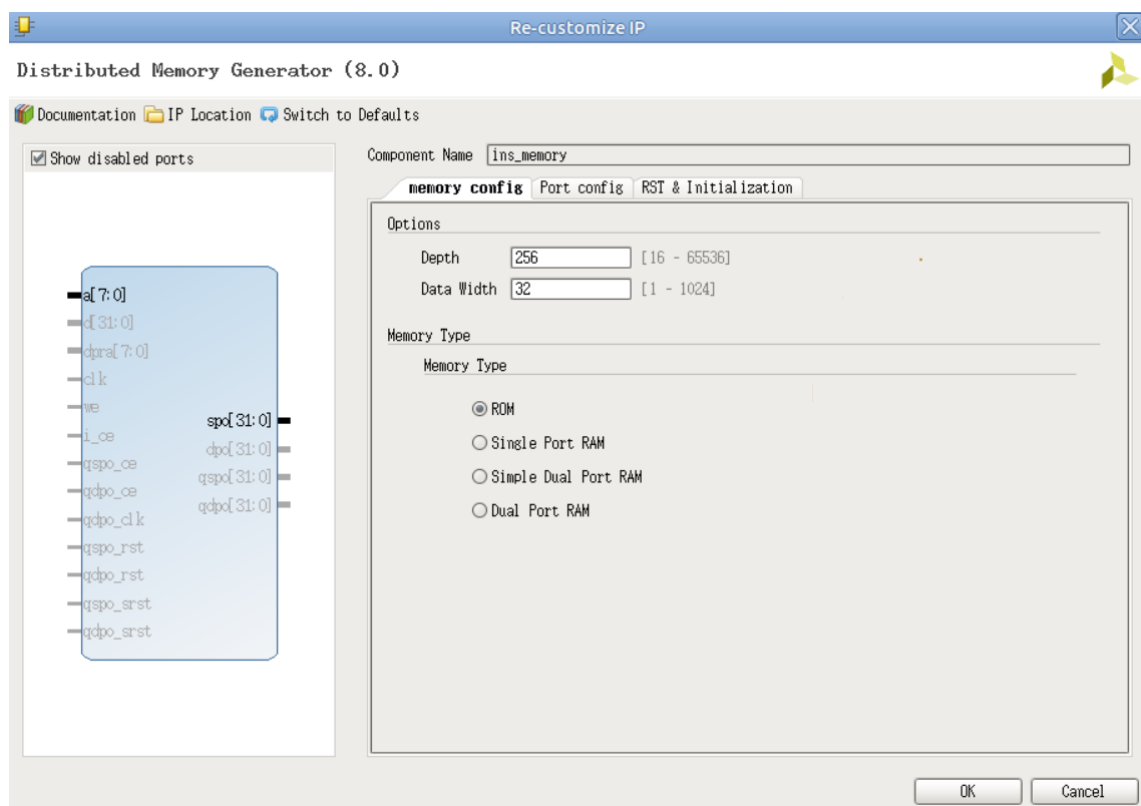
## ⑥data\_memory & ins\_memory

分别使用两个分布式存储器ip核，并用对应的data.coe和ins.coe文件对其进行初始化；



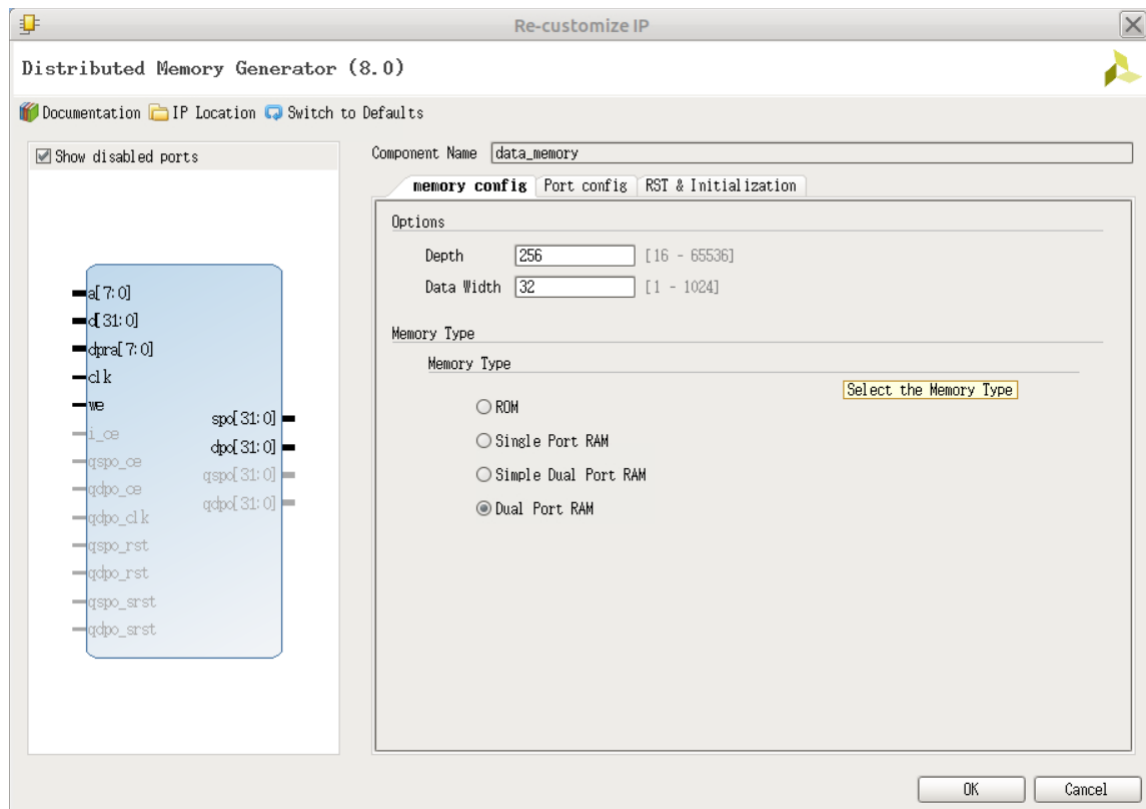

## ⑦CPU主体模块

```

1  module cpu(
2  input clk,rst,
3  input [31:0] io_din,
4  input [7:0] m_rf_addr ,
5  output [7:0] io_addr ,
6  output [31:0] io_dout ,
7  output io_we ,
8  output [31:0] rf_data,
9  output [31:0] m_data ,
10 output reg [31:0] pc
11 );
12
13 wire Zero;
14 wire Branch,MemRead,MemWrite,ALUSrc,RegWrite,JUMP,jalr_PC,auipc;
15 wire MemWrite_true;
16 wire [1:0] ALUOp ,MemtoReg;
17 wire [31:0] ins, imm;
18 wire [31:0] readData1,readData2,ALU_input2,ALU_input1;
19 wire [31:0] Mem_ReadData, RF_writeData;
20 wire [31:0] Mem_ReadData_waishe, Mem_ReadData_MEM;
21 wire [31:0] npc_4,PC_offset,PC_jalr,PC_mux;
22 wire [31:0] npc;
23 wire which_PC;
24 wire [31:0] ALU_result;
25 reg [31:0] writeData;
26 wire [2:0] sel;
27 wire [31:0] io_addr1;
28 wire [7:0] apc;
29
30 ins_memory IMem(.a(apc),.spo(ins));

```

```

31     data_memory
32     DMem(.a(ALU_result[9:2]),.d(readData2),.dpra(m_rf_addr),.clk(clk),.we(Memwrite_true),.spo(Mem_ReadData_MEM),.dpo(m_data));
33
34 control control(.ins(ins),
35 .ALUSrc(ALUSrc),.RegWrite(RegWrite),.MemRead(MemRead),
36 .MemWrite(MemWrite),.Branch(Branch),.JUMP(JUMP),.jalr_PC(jalr_PC),.auipc(auipc),
37 .ALUOp(ALUOp), .MemtoReg(MemtoReg) );
38
39 rf #(.m(5),.WIDTH(32)) rf (.clk(clk),.we(RegWrite),
40 .wa(ins[11:7]),.ra0(ins[19:15]),.ra1(ins[24:20]),
41 .wd(writeData),.rd0(readData1),.rd1(readData2),
42 .rf_addr(m_rf_addr[4:0]),
43 .rf_data(rf_data),.rst(rst));
44
45 immg immg(.ins(ins),.imm(imm));
46
47 alu_control alu_control(.aluop(ALUOp),.sel(sel));
48
49 alu # (32)
50 alu(.a(ALU_input1),.b(ALU_input2),.ins(ins),.f(sel),.z(Zero),.y(ALU_result))
51 ;
52
53 assign PC_jalr = ALU_result & (~32'b1); //jalr PC
54 assign npc_4 = pc + 4; //pc+4
55 assign PC_offset = pc + imm;
56 assign which_PC = (Branch & Zero) | JUMP ;
57 assign PC_mux = which_PC ? PC_offset : npc_4;
58 assign npc = jalr_PC ? PC_jalr : PC_mux;
59 assign ALU_input2 = ALUSrc ? imm : readData2;
60 assign ALU_input1 = auipc ? pc : readData1;
61 assign apc = pc[9:2];
62
63 always@(posedge clk or posedge rst)
64 begin
65     if(rst) pc <= 32'h0000_3000;
66     else pc <= npc;
67 end
68
69 //register file writedata
70 always@(*)
71 begin
72     if((JUMP==0)|| (jalr_PC==0))
73     begin
74         if(MemtoReg==0) writeData = ALU_result;
75         else writeData = Mem_ReadData;
76     end
77     else writeData = npc_4 ;
78 end
79
80 assign io_addr1=ALU_result;
81 assign io_addr = io_addr1[7:0];
82 assign MemWrite_true = (~io_addr1[10]) & MemWrite;
83 assign Mem_ReadData_waishe = io_din;
84 assign Mem_ReadData = io_addr1[10]? Mem_ReadData_waishe : Mem_ReadData_MEM;
85 assign io_dout = readData2;
86 assign io_we = io_addr1[10] & MemWrite;
87

```



## 2.pdu模块 (用于io)

```

1  module pdu(
2      input clk,
3      input rst,
4
5      //选择CPU工作方式;
6      input run,
7      input step,
8      output clk_cpu,
9
10     //输入switch的端口
11     input valid,
12     input [4:0] in,
13
14     //输出led和seg的端口
15     output [1:0] check, //led6-5:查看类型
16     output [4:0] out0, //led4-0
17     output [2:0] an, //8个数码管
18     output [3:0] seg,
19     output ready, //led7
20
21     //IO_BUS
22     input [7:0] io_addr,
23     input [31:0] io_dout,
24     input io_we,
25     output [31:0] io_din,
26
27     //Debug_BUS
28     output [7:0] m_rf_addr,
29     input [31:0] rf_data,
30     input [31:0] m_data,
31     input [31:0] pc
32 );
33
34 reg [4:0] in_r; //同步外部输入用
35 reg run_r, step_r, step_2r, valid_r, valid_2r;
36 wire step_p, valid_pn; //取边沿信号
37
38 reg clk_cpu_r; //寄存器输出CPU时钟
39 reg [4:0] out0_r; //输出外设端口
40 reg [31:0] out1_r;
41 reg ready_r;
42 reg [19:0] cnt; //刷新计数器，刷新频率约为95Hz
43 reg [1:0] check_r; //查看信息类型，00-运行结果，01-寄存器堆，10-存储器，11-PC
44
45 reg [7:0] io_din_a; //_a表示为满足组合always描述要求定义的，下同
46 reg ready_a;
47 reg [4:0] out0_a;
48 reg [31:0] out1_a;
49 reg [3:0] seg_a;
50
51 assign clk_cpu = clk_cpu_r;

```

```

52 assign io_din = io_din_a;
53 assign check = check_r;
54 assign out0 = out0_a;
55 assign ready = ready_a;
56 assign seg = seg_a;
57 assign an = cnt[19:17];
58 assign step_p = step_r & ~step_2r;      //取上升沿
59 assign valid_pn = valid_r ^ valid_2r;    //取上升沿或下降沿
60 assign m_rf_addr = {{3{1'b0}}, in_r};
61
62 //同步输入信号
63 always @(posedge clk) begin
64     run_r <= run;
65     step_r <= step;
66     step_2r <= step_r;
67     valid_r <= valid;
68     valid_2r <= valid_r;
69     in_r <= in;
70 end
71
72 //CPU工作方式
73 always @(posedge clk, posedge rst) begin
74     if(rst)
75         clk_cpu_r <= 0;
76     else if (run_r)
77         clk_cpu_r <= ~clk_cpu_r;
78     else
79         clk_cpu_r <= step_p;
80 end
81
82 //读外设端口
83 always @* begin
84     case (io_addr)
85         8'h0c: io_din_a = {{27{1'b0}}, in_r};
86         8'h10: io_din_a = {{31{1'b0}}, valid_r};
87         default: io_din_a = 32'h0000_0000;
88     endcase
89 end
90
91 //写外设端口
92 always @(posedge clk, posedge rst) begin
93     if (rst) begin
94         out0_r <= 5'h1f;
95         out1_r <= 32'h1234_5678;
96         ready_r <= 1'b1;
97     end
98     else if (io_we)
99         case (io_addr)
100             8'h00: out0_r <= io_dout[4:0];
101             8'h04: ready_r <= io_dout[0];
102             8'h08: out1_r <= io_dout;
103             default: ;
104         endcase
105     end
106
107 //LED和数码管查看类型
108 always @(posedge clk, posedge rst) begin
109     if(rst)

```

```

110     check_r <= 2'b00;
111     else if(run_r)
112         check_r <= 2'b00;
113     else if (step_p)
114         check_r <= 2'b00;
115     else if (valid_pn)
116         check_r <= check - 2'b01;
117 end
118
119 //LED和数码管显示内容
120 always @* begin
121     ready_a = 1'b0;
122     case (check_r)
123         2'b00: begin
124             out0_a = out0_r;
125             out1_a = out1_r;
126             ready_a = ready_r;
127         end
128         2'b01: begin
129             out0_a = in_r;
130             out1_a = rf_data;
131         end
132         2'b10: begin
133             out0_a = in_r;
134             out1_a = m_data;
135         end
136         2'b11: begin
137             out0_a = 5'b00000;
138             out1_a = pc;
139         end
140     endcase
141 end
142
143 //扫描数码管
144 always @(posedge clk, posedge rst) begin
145     if (rst) cnt <= 20'h0_0000;
146     else cnt <= cnt + 20'h0_0001;
147 end
148
149 always @* begin
150     case (an)
151         3'd0: seg_a = out1_a[3:0];
152         3'd1: seg_a = out1_a[7:4];
153         3'd2: seg_a = out1_a[11:8];
154         3'd3: seg_a = out1_a[15:12];
155         3'd4: seg_a = out1_a[19:16];
156         3'd5: seg_a = out1_a[23:20];
157         3'd6: seg_a = out1_a[27:24];
158         3'd7: seg_a = out1_a[31:28];
159         default: ;
160     endcase
161 end
162
163 endmodule

```

(1) 外设使用说明：

外设使用说明表

sw				button	led			an/seg	说明
7	6	5	4~0		7	6~5	4~0		
rst	run	valid	in	step	ready	check	out0	out1	
↑	-	-	-	-	1	00	0x1f	0x12...8	复位
x	1	valid	in	-	ready	00	out0	out1	连续运行
	0	valid	in	↑	ready	00	out0	out1	单步运行
		↑↓	addr_rf	x	0	01	addr_rf	data_rf	查看寄存器堆
			addr_m		0	10	addr_m	data_m	查看存储器
			-		0	11	0	PC	查看PC

(2) 存储器配置：

实验存储器配置

- 指令存储器(256x32bit)地址： 0x0000\_3000 ~ 0x0000\_33ff
- 数据存储器(256x32bit)地址： 0x0000\_0000 ~ 0x0000\_03ff
- 外设端口地址： 0x0000\_0400 ~ 0x0000\_07ff

存储器映射外设端口地址表

存储器地址	I/O_addr	输出端口名	输入端口名	外设
0x0000_0400	0	out0	-	led4-0
0x0000_0404	1	ready	-	led7
0x0000_0408	2	out1	-	an, seg
0x0000_040C	3	-	in	sw4-0
0x0000_0410	4	-	valid	sw5

3.10条指令测试汇编程序以及仿真

(1) 汇编程序

```
1 .data
2 0x400
3 0xfe
4
5 .text
6 lw t3, 0(x0)
7 sw x0, 8(t3)           #test sw
8 addi t0, x0, 0xff      #test addi
```

```

9  sw t0, 8(t3)
10 lw t0, 4(x0)           #test lw
11 sw t0, 8(t3)
12 addi t1,x0,1
13 add t0,t1,t0           #test add
14 sw t0, 8(t3)           #t0=t0+t1
15 sub t0,t0,t1           #t0=t0-t1, test sub
16 sw t0, 8(t3)
17 addi t2,x0,1
18 auipc t1,0             #test auipc
19 loop1:
20 blt t2,x0,be           #test blt
21 addi t2,t2,-1
22 sw t2, 8(t3)
23 jalr x1,t1,4           #test jalr
24 be: addi t2,x0,1
25 loop:
26 beq t2,x0,exit         #test beq
27 addi t2,t2,-1
28 sw t2, 8(t3)
29 jal x1,loop            #test jal
30 exit:

```

## (2) 仿真文件

```



1  module cpu_sim(
2  );
3  reg clk;
4  reg rst;
5  reg [31:0] io_din;
6  reg [7:0] m_rf_addr;
7
8  initial clk = 0;
9  always #5 clk = ~clk;
10 initial rst = 1;
11 initial #10 rst = 0;
12 initial m_rf_addr = 1;
13 initial io_din = 0;
14 initial #300 $stop;
15
16 cpu cpu1(.clk(clk),.rst(rst),.m_rf_addr(m_rf_addr),.io_din(io_din));
17
18 endmodule

```

## (3) 仿真截图



## FPGA interface

 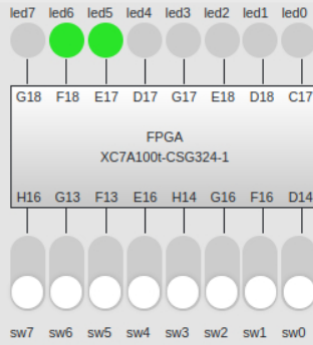

uart pins: cts rts rxd txd  
xdc,ucf sym: D3 E5 D4 C4

segplay(sharing with led) hexplay



segplay pin: dot seg\_g seg\_f seg\_e seg\_d seg\_c seg\_b seg\_a  
xdc,ucf sym: G18 F18 E17 D17 G17 E18 D18 C17  
hexplay pin: an2 an1 an0 d3 d2 d1 d0



soft clock

button

None

clk btn pins: clk\_btn  
xdc,ucf sym: B18

## FPGA interface

 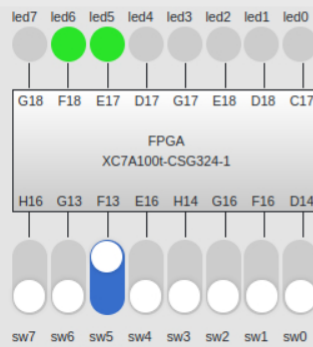

uart pins: cts rts rxd txd  
xdc,ucf sym: D3 E5 D4 C4

segplay(sharing with led) hexplay



segplay pin: dot seg\_g seg\_f seg\_e seg\_d seg\_c seg\_b seg\_a  
xdc,ucf sym: G18 F18 E17 D17 G17 E18 D18 C17  
hexplay pin: an2 an1 an0 d3 d2 d1 d0



soft clock

button

None

clk btn pins: clk\_btn  
xdc,ucf sym: B18

## FPGA interface

  

uart pins: cts rts rxd txd  
xdc,ucf sym: D3 E5 D4 C4

segplay(sharing with led) hexplay



segplay pin: dot seg\_g seg\_f seg\_e seg\_d seg\_c seg\_b seg\_a  
xdc,ucf sym: G18 F18 E17 D17 G17 E18 D18 C17  
hexplay pin: an2 an1 an0 d3 d2 d1 d0

soft clock

button

None

clk btn pins: clk\_btn  
xdc,ucf sym: B18

## 5.fib仿真

### (1) 仿真文件


```

1  module top_sim(
2      );
3
4  reg clk,rst,run,valid,step;
5  reg [4:0] in;
6  wire [1:0] check;
7  wire [4:0] out0;
8  wire [2:0] an;
9  wire [3:0] seg;
10 wire ready;
11
12 top top1(.clk(clk),.rst(rst),.run(run),.valid(valid),.step(step),.in(in),
13 .check(check),.out0(out0),.an(an),.seg(seg),.ready(ready));
14
15 initial clk = 0;
16 always #4 clk = ~clk;
17 initial valid = 0;
18 always #7 valid = ~valid;
19 initial
20 begin
21     rst = 1;run = 0; in = 0; step = 0;
22     #20 rst = 0;
23     #2 run=1;
24     #5 in = 1;
25     #250 in = 2;
26     #600 $finish;
27 end
28
29 endmodule

```



### (2) 仿真截图

输入前两项为1和2, 后面自动输出3, 5, 8 .....


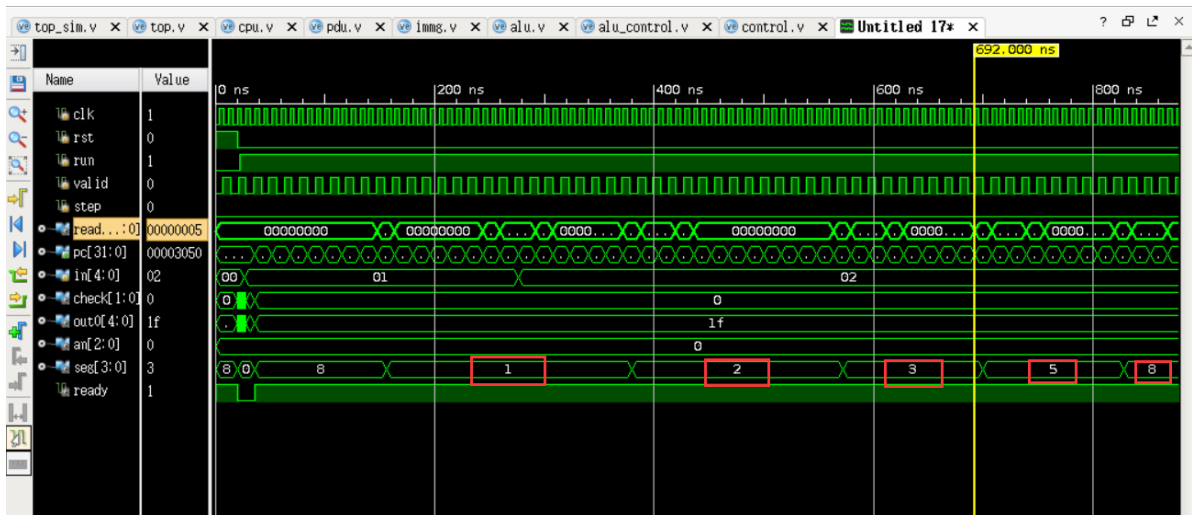




## 6.fib上板（fpga平台测试）

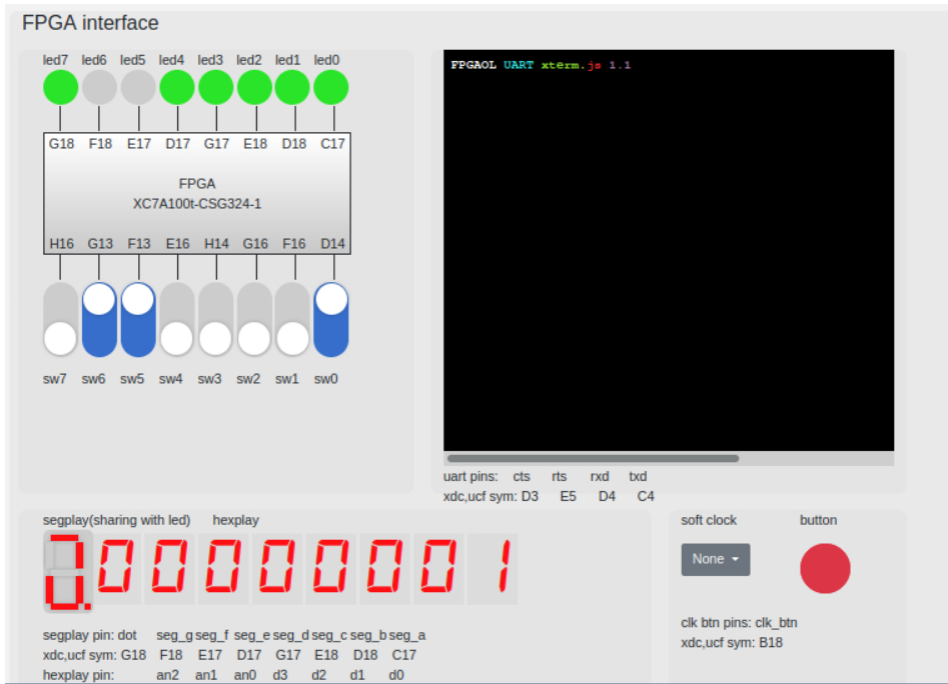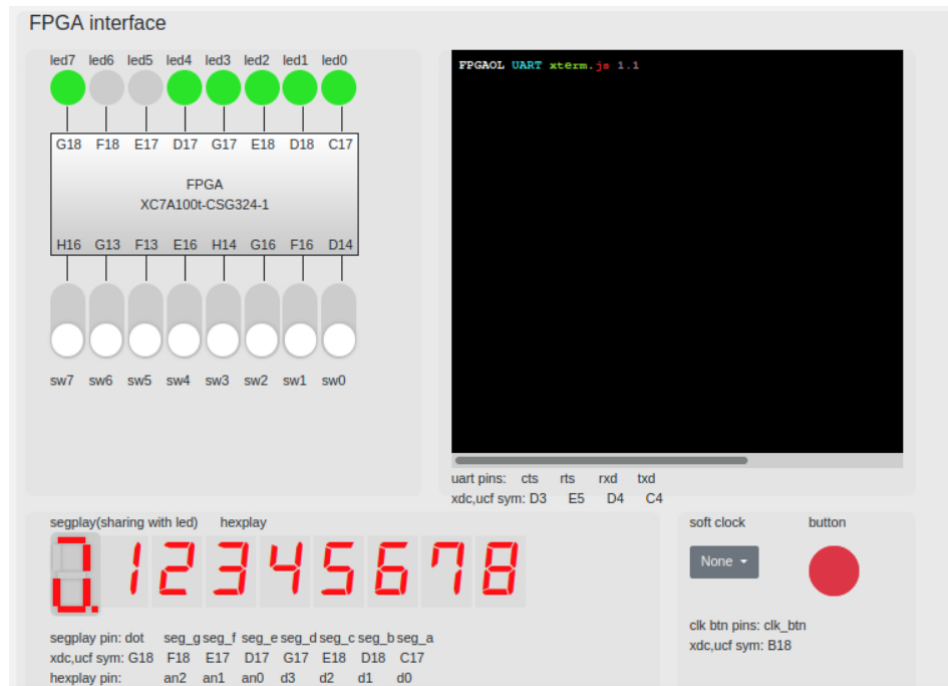

### FPGA interface

  

uart pins: cts rts rxd bxd  
xdc,ucf sym: D3 E5 D4 C4

segplay(sharing with led) hexplay

000000002



segplay pin: dot seg\_g seg\_f seg\_e seg\_d seg\_c seg\_b seg\_a  
xdc,ucf sym: G18 F18 E17 D17 G17 E18 D18 C17  
hexplay pin: an2 an1 an0 d3 d2 d1 d0

soft clock button

None

clk btn pins: clk\_btn  
xdc,ucf sym: B18

### FPGA interface

 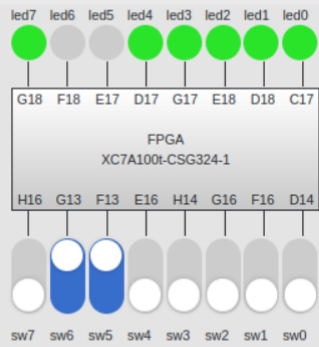

uart pins: cts rts rxd bxd  
xdc,ucf sym: D3 E5 D4 C4

segplay(sharing with led) hexplay

000000003



segplay pin: dot seg\_g seg\_f seg\_e seg\_d seg\_c seg\_b seg\_a  
xdc,ucf sym: G18 F18 E17 D17 G17 E18 D18 C17  
hexplay pin: an2 an1 an0 d3 d2 d1 d0

soft clock button

None

clk btn pins: clk\_btn  
xdc,ucf sym: B18

### FPGA interface

  

uart pins: cts rts rxd bxd  
xdc,ucf sym: D3 E5 D4 C4

segplay(sharing with led) hexplay

000000005

segplay pin: dot seg\_g seg\_f seg\_e seg\_d seg\_c seg\_b seg\_a  
xdc,ucf sym: G18 F18 E17 D17 G17 E18 D18 C17  
hexplay pin: an2 an1 an0 d3 d2 d1 d0

soft clock button

None

clk btn pins: clk\_btn  
xdc,ucf sym: B18

